

# mmWave Phase Interpolators

Architectures for phase control and generation for V/E Bands

---

Rahul Narwar

HIE Lab, University of California, Irvine

# First Principles


---

# What is a Phase Interpolator?

A circuit that produces a clock at **any phase between two reference phases** by taking a weighted sum.

- **Inputs:** two reference clocks, same frequency, known phase offset (typically  $90^\circ$  apart — I and Q)
- **Control:** digital code  $\rightarrow$  analog weights  $(\alpha, \beta)$
- **Output:** one clock with phase  $\phi \in [\phi_I, \phi_Q]$ , same frequency

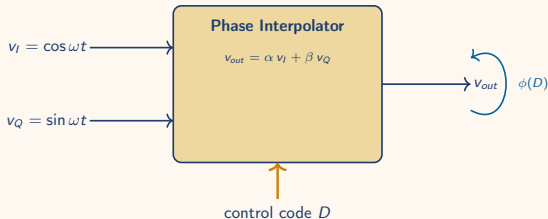No frequency synthesis, no PLL — *just controlled mixing of two phases.*



*Black box: 2 phases in, 1 phase out, code controls where.*

Given two orthogonal clocks at  $\omega$ :

$$v_I(t) = A \cos \omega t, \quad v_Q(t) = A \sin \omega t.$$

Take a weighted sum with real weights  $\alpha, \beta$ :


$$v_{out}(t) = \alpha v_I(t) + \beta v_Q(t) = A[\alpha \cos \omega t + \beta \sin \omega t].$$

Apply the harmonic-addition identity  $a \cos \theta + b \sin \theta = R \cos(\theta - \phi)$  with  $R = \sqrt{a^2 + b^2}$ ,  $\tan \phi = b/a$ :

$$v_{out}(t) = A \sqrt{\alpha^2 + \beta^2} \cos(\omega t - \phi), \quad \phi = \arctan \frac{\beta}{\alpha}.$$
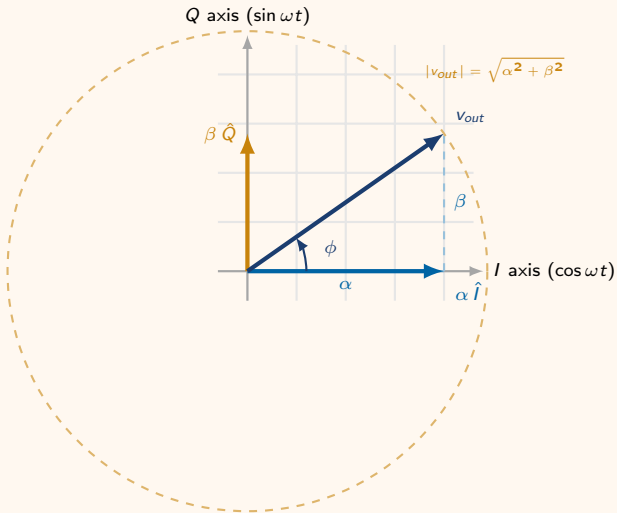
## Takeaway

The output *frequency* is unchanged. The output *phase* is set entirely by the weight ratio  $\beta/\alpha$  — sweep the weights, sweep the phase from  $0^\circ$  (pure I) to  $90^\circ$  (pure Q).




## Two knobs:

- **Quadrant select** (coarse) — pick two of  $\{I, Q, \bar{I}, \bar{Q}\}$  for  $360^\circ$  coverage
- **Weight ratio** (fine) —  $N$ -bit DAC on  $\beta/\alpha$  gives  $2^N$  steps per quadrant

# Phased-Array Beam Steering

---

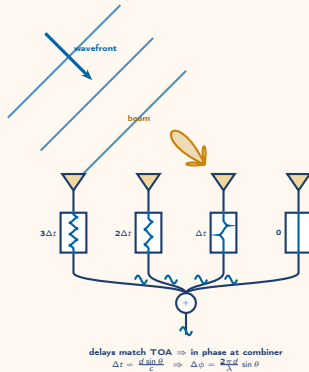

**Idea.** Feed each antenna the *same signal* but with a progressive phase shift  $\Delta\phi$  between neighbours. The array radiates a beam at angle

$$\sin \theta = \frac{\lambda}{2\pi d} \Delta\phi.$$

Change  $\Delta\phi$  electronically  $\rightarrow$  steer  $\theta$  with no moving parts.

**Why a PI per element?**

- Continuous, monotonic phase
- Per-element skew calibration
- Same hardware across the band — only  $\Delta\phi$  changes

**Array equation** ( $d$  spacing,  $\lambda$  wavelength). Differentiate to map small  $\Delta\phi$  to small  $\Delta\theta$ :

$$\Delta\phi = \frac{2\pi d}{\lambda} \sin \theta \implies \boxed{\Delta\theta = \frac{\lambda}{2\pi d \cos \theta} \Delta\phi_{\min}}$$

For an  $N$ -bit PI ( $\Delta\phi_{\min} = 2\pi/2^N$ ) at the typical half-wavelength spacing  $d = \lambda/2$ :  
 $\Delta\theta = (1/\cos \theta) \cdot 2^{-(N-1)}$  rad.

| $N$ | $\Delta\phi_{\min}$ | $\Delta\theta_{@0^\circ}$ | $\Delta\theta_{@60^\circ}$ |
|-----|---------------------|---------------------------|----------------------------|
| 4   | 22.5°               | 7.2°                      | 14.3°                      |
| 6   | 5.6°                | 1.8°                      | 3.6°                       |
| 8   | 1.4°                | 0.45°                     | 0.90°                      |




## Wireline / SerDes

---

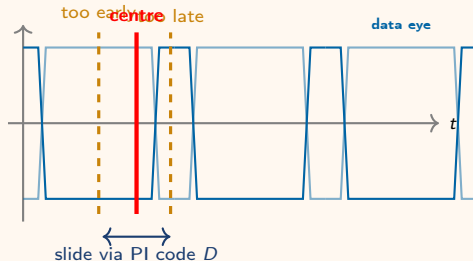**Problem.** Receiver gets serial data with no clock. Local reference clock is at the right *frequency* but unknown *phase*.


**PI's job.** Slide the sampling clock until it lands in the *centre of the data eye* — and keep it there as the link drifts.

$$\phi_{samp} = \frac{1}{2}(\phi_{rise} + \phi_{fall})$$



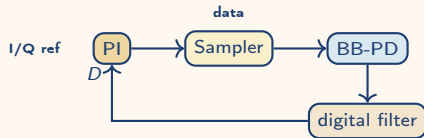
## Why a PI?

Resolution of  $360^\circ/2^N$  at multi-GHz rates with no PLL in the loop. A bang-bang phase detector dithers the PI code  $\pm 1$  LSB at lock — the entire CDR loop is digital after the sampler.



## Proposed Architecture

---

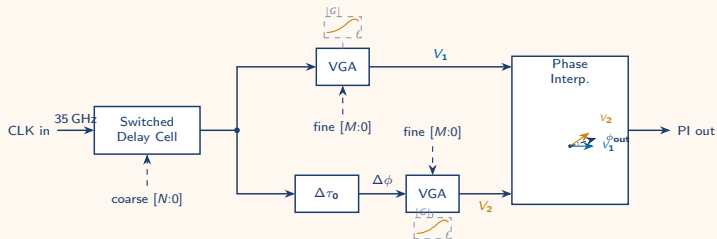

## Design parameters:

- $f_{in} = 35$  GHz, BW 30–40 GHz
- **Coarse**  $[N:0]$ : selects boundary phasors via switched delay
- **Fine**  $[M:0]$ : sets VGA weight ratio  $(\alpha, \beta)$
- $\Delta\tau_0$  fixes phasor gap  $\Delta\phi = \omega\Delta\tau_0$
- VGA gain peaks toward band edge (broadband equalization)
- Output:  $\phi = \arctan(\beta/\alpha)$

Questions?